

---

## Using PWM to Generate an Analog Output

---

### Introduction

---

A wide variety of microcontroller applications require the use of analog output signals. Many low-cost microcontrollers have peripherals to process analog input signals, such as an Analog-to-Digital Converter (ADC), but often do not have a Digital-to-Analog Converter (DAC) included. Of course, there are options for external DACs; however, those may require extra I/O connections or PCB space, and will add cost to the application. Fortunately, most microcontrollers offer a Pulse-Width Modulation (PWM) module, which can be combined with a low-pass filter to create an analog output. This technical brief highlights the use of a low-pass filter to transform a PWM signal into an analog signal.

---

## Table of Contents


---

Introduction.....	1
1. Pulse-Width Modulation (PWM).....	3
1.1. Configuring the PWM Module.....	3
2. Low-Pass Filtering.....	5
2.1. RC Filter Example.....	6
3. Conclusion.....	14
The Microchip Website.....	15
Product Change Notification Service.....	15
Customer Support.....	15
Microchip Devices Code Protection Feature.....	15
Legal Notice.....	15
Trademarks.....	16
Quality Management System.....	16
Worldwide Sales and Service.....	17

## 1. Pulse-Width Modulation (PWM)

PWM modules generate pulse-width modulated digital signals. In a typical PWM signal, the base frequency is fixed, while the pulse-width is variable (see [Figure 1-1](#)). The pulse-width, also referred to as duty cycle, is directly proportional to the amplitude of the original unmodulated signal as shown in [Equation 1-1](#). For example, if a 2.5V output signal is desired, and the PWM signal has a logic high voltage of 5V and a logic low of 0V, a PWM signal with a duty cycle of 50% will suffice. A 50% duty cycle means that for half of the period, the PWM outputs 5V and the average output per period is 2.5V.

**Figure 1-1. PWM Waveform**

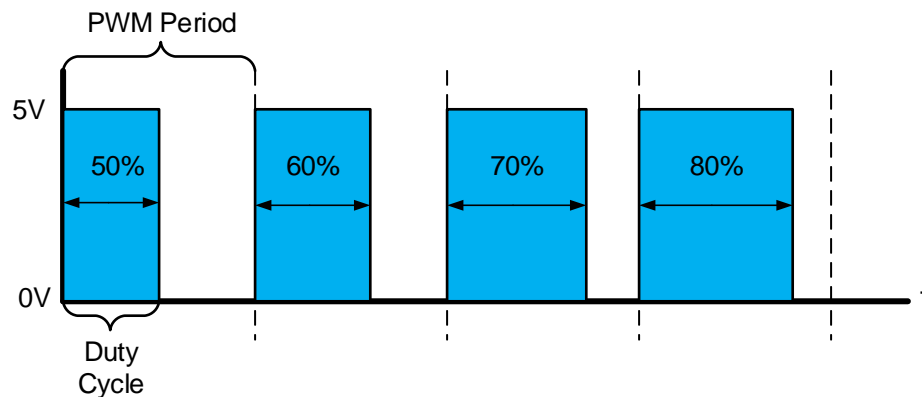

### Equation 1-1. Voltage Output

$$V_{OUT} = A \times \text{Duty Cycle}$$

where:

$A$  = Logic 'high' voltage amplitude

### 1.1 Configuring the PWM Module

[Example 1-1](#) shows how to configure a standard 10-bit PWM. The example includes the initialization routines for the PWM and Timer2 modules, both of which are necessary to generate a PWM signal.

**Example 1-1. PWM and Timer2 Initialization Routines**

```
void PWM3_Initialize(void)
{
    PWM3CON = 0x80;           // POL active_hi; EN enabled
    PWM3DCH = 0x27;           // DC = 50%
    PWM3DCL = 0xC0;
}


void PWM3_LoadDutyValue(uint16_t dutyValue)
{
    PWM3DCH = (dutyValue & 0x03FC)>>2; // 8 MSBs of PWM duty cycle
    PWM3DCL = (dutyValue & 0x0003)<<6; // 2 LSBs of PWM duty cycle
}

void TMR2_Initialize(void)
{
    T2CLKCON = 0x01;          // T2CS FOSC/4
    T2HLT = 0x00;
    T2RST = 0x00;
    T2PR = 0x4F;              // Rollover every 10 us
    T2TMR = 0x00;
    PIR4bits.TMR2IF = 0;      // Clear IF flag
    T2CON = 0x80;             // CKPS 1:1; OUTPS 1:1; ON on
}
```

## 2. Low-Pass Filtering

A Fourier analysis of a typical PWM signal shows a peak at the carrier frequency, with higher order harmonics present at the integer multiples of the carrier (see Figure 2-1). These signals add unwanted noise to the system and can be reduced or eliminated using a simple low-pass filter.

Figure 2-1. Fourier Analysis of a PWM Signal

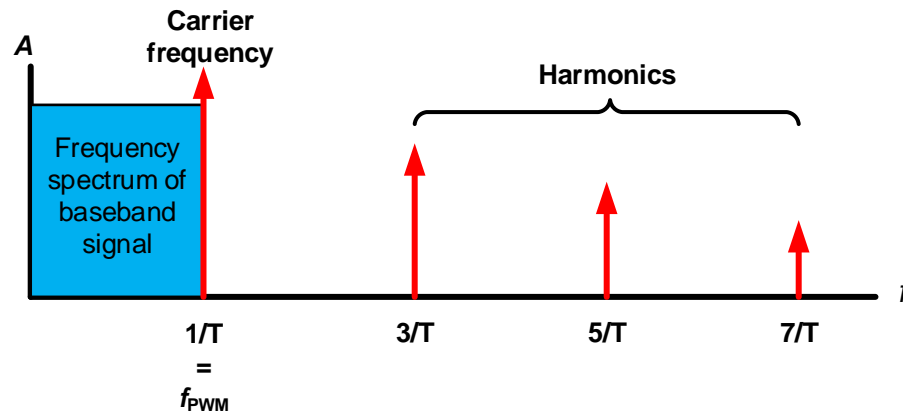

The bandwidth of the desired signal should be less than or equal to the PWM frequency (see Figure 2-2). If the bandwidth of the desired signal is equal to the PWM frequency, a brick-wall type of filter may be used. The brick-wall type of filter transitions from no attenuation to complete attenuation almost instantly, but is a very expensive and complex filter to create. If that type of precision is necessary, it might be less expensive to use an external DAC than to build an expensive filter. For practical purposes, an external RC low-pass filter can be used as shown in Figure 2-3. If the simple RC filter is used, the bandwidth of the desired signal must be less than the PWM frequency.

Figure 2-2. Desired Bandwidth of a PWM Signal


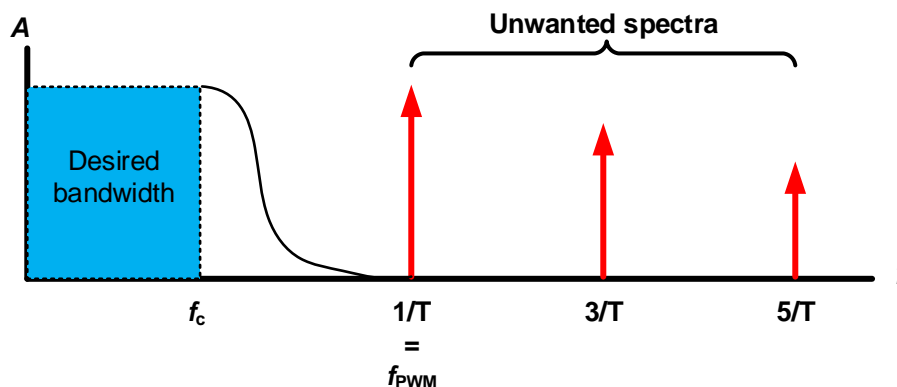


Figure 2-3. External RC Low-Pass Filter

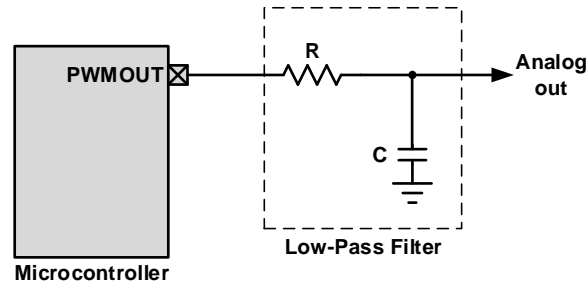

## 2.1 RC Filter Example

For this example, it is required to design a simple RC low-pass filter to obtain an analog output from a pulse-width modulated signal with a bandwidth of 4 kHz.

**Step 1: Select the low-pass filter's resistor and capacitor values.**

Equation 2-1 shows how to calculate the values for R and C based on the cut-off frequency,  $f_C$ . In this example, the resistor values were calculated based on fixed capacitor values, as shown in Table 2-1.

**Equation 2-1. RC Time Constant**

$$RC = \frac{1}{2\pi \times f_C}$$

where:

R: Resistance

C: Capacitance

$f_C$ : cut-off frequency

Table 2-1. Calculated Resistor Values

Capacitor Value	Calculated Resistor Value
1 pF	40 MΩ
0.01 μF	4 kΩ
0.022 μF	1.8 kΩ

**Step 2: Calculate attenuation at the PWM frequency.**

Equation 2-2 shows the attenuation in decibels (dB) based on the RC values and the PWM frequency.

**Equation 2-2. Attenuation in Decibels (dB)**


$$\text{Attenuation (dB)} @ f_{PWM} = -10\log\left[1 + (2\pi \times f_{PWM} \times RC)^2\right]$$

Table 2-2. Attenuation at the PWM Frequency ( $F_{PWM}$ )


$F_{PWM}$	R Value	C Value	Attenuation (dB) @ $F_{PWM}$
10 kHz	40 MΩ	1 pF	-8.64
10 kHz	4 kΩ	0.01 μF	-8.64

.....continued			
$F_{PWM}$	R Value	C Value	Attenuation (dB) @ $F_{PWM}$
10 kHz	1.8 k $\Omega$	0.022 $\mu$ F	-8.57
100 kHz	40 M $\Omega$	1 pF	-28.01
100 kHz	4 k $\Omega$	0.01 $\mu$ F	-28.01
100 kHz	1.8 k $\Omega$	0.022 $\mu$ F	-27.92


**Figure 2-4. Bode Plot**

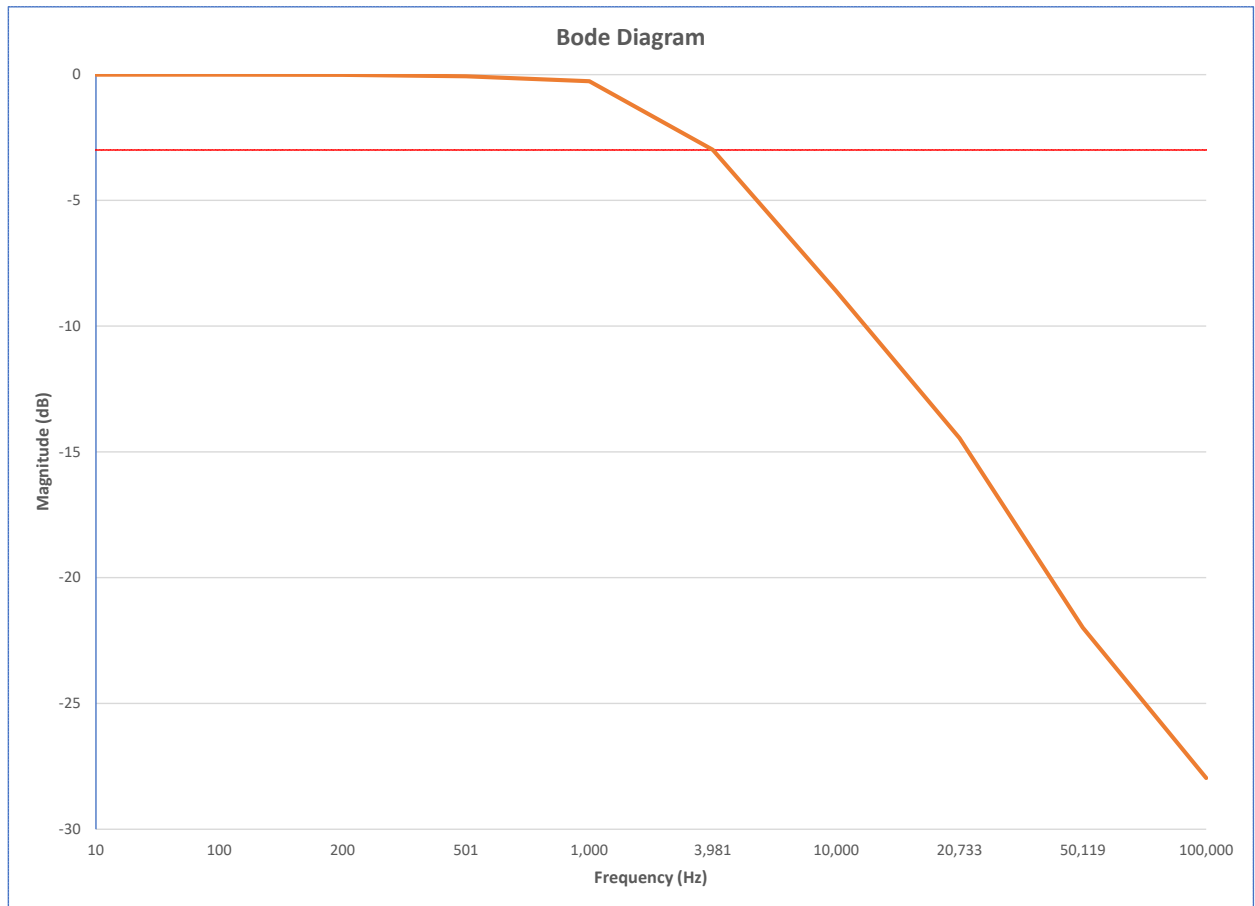


**Figure 2-5. Step Response ( $R = 40\text{ M}\Omega$ ,  $C = 1\text{ pF}$ ,  $F_{\text{PWM}} = 10\text{ kHz}$ )**

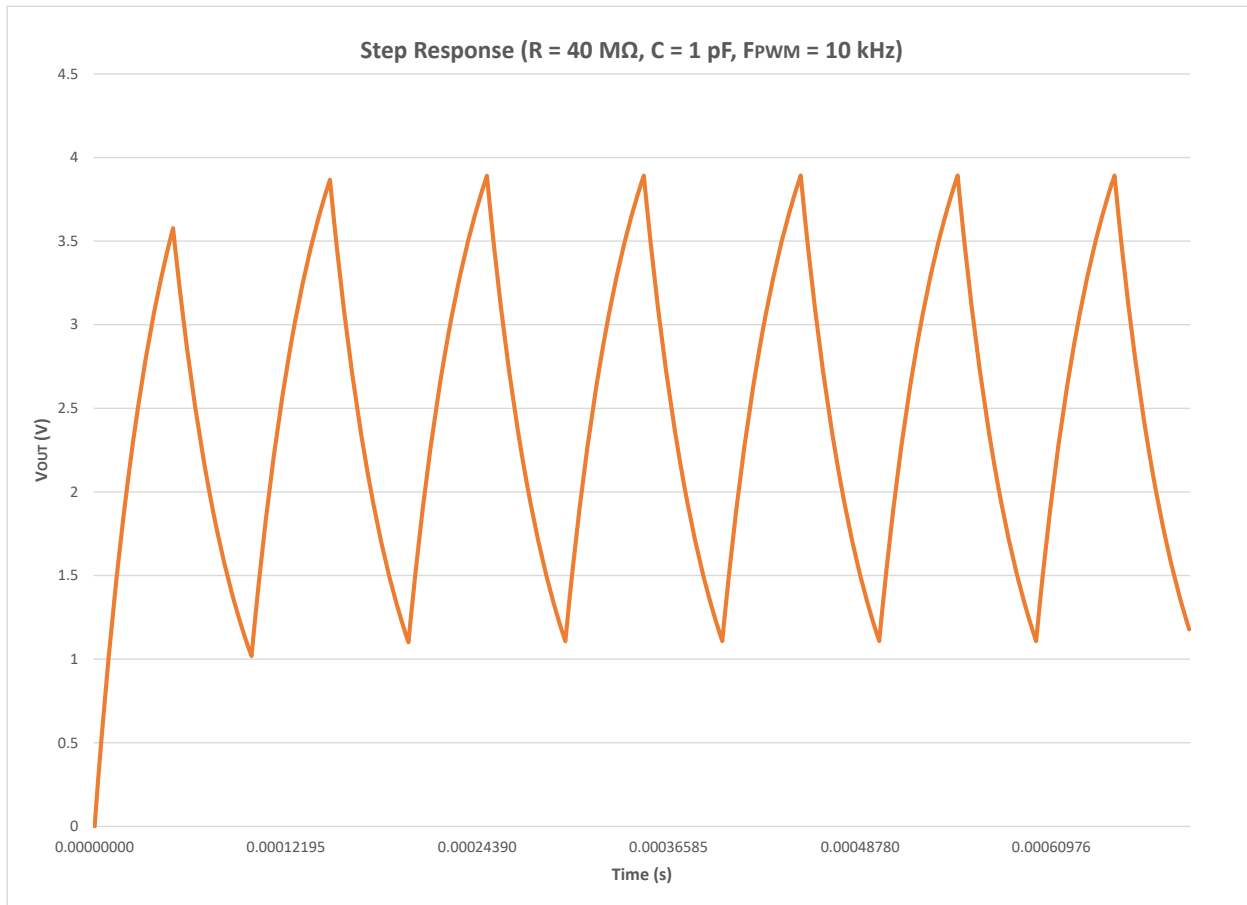


**Figure 2-6. Step Response ( $R = 40\text{ M}\Omega$ ,  $C = 1\text{ pF}$ ,  $F_{\text{PWM}} = 100\text{ kHz}$ )**

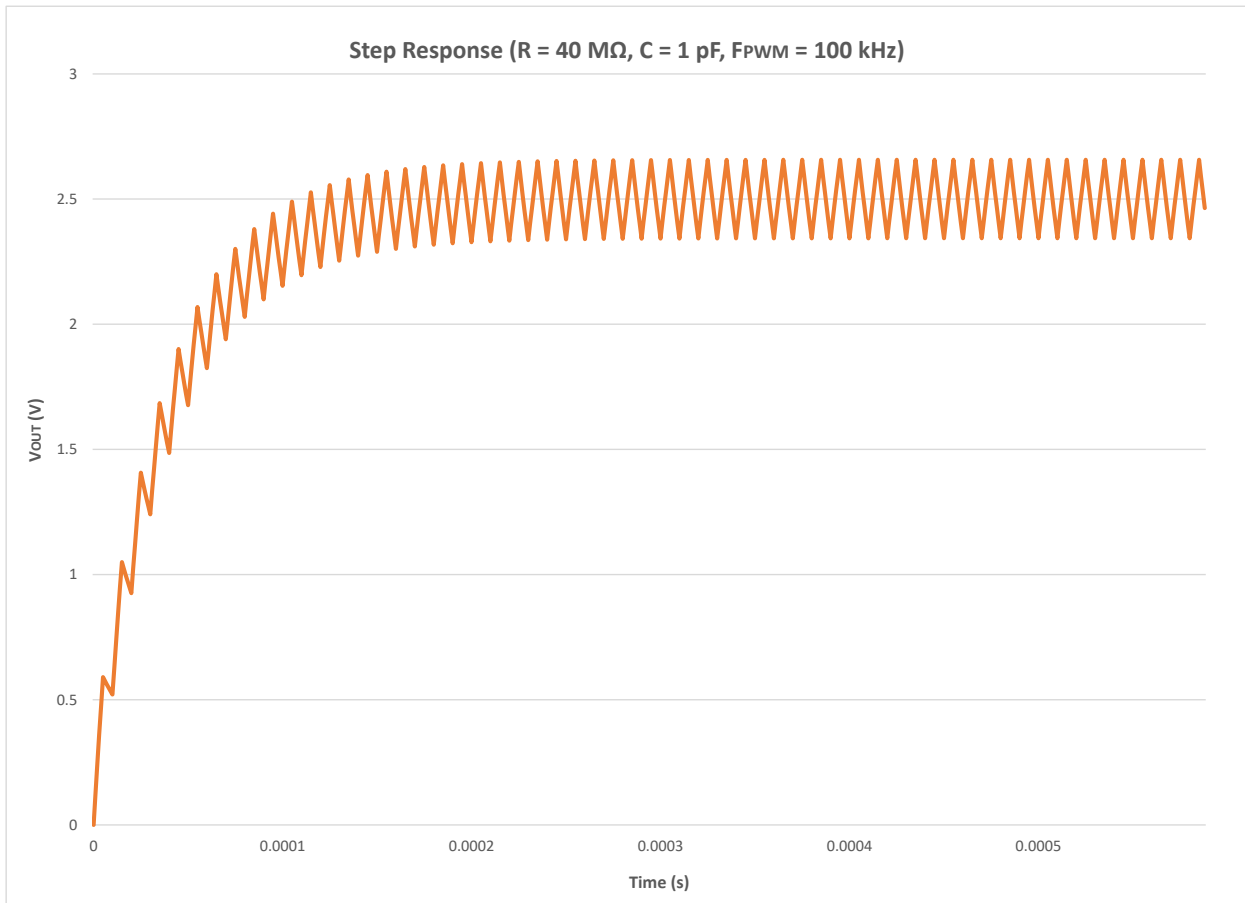

**Figure 2-7. Step Response ( $R = 4\text{ k}\Omega$ ,  $C = 0.01\text{ }\mu\text{F}$ ,  $F_{\text{PWM}} = 10\text{ kHz}$ )**

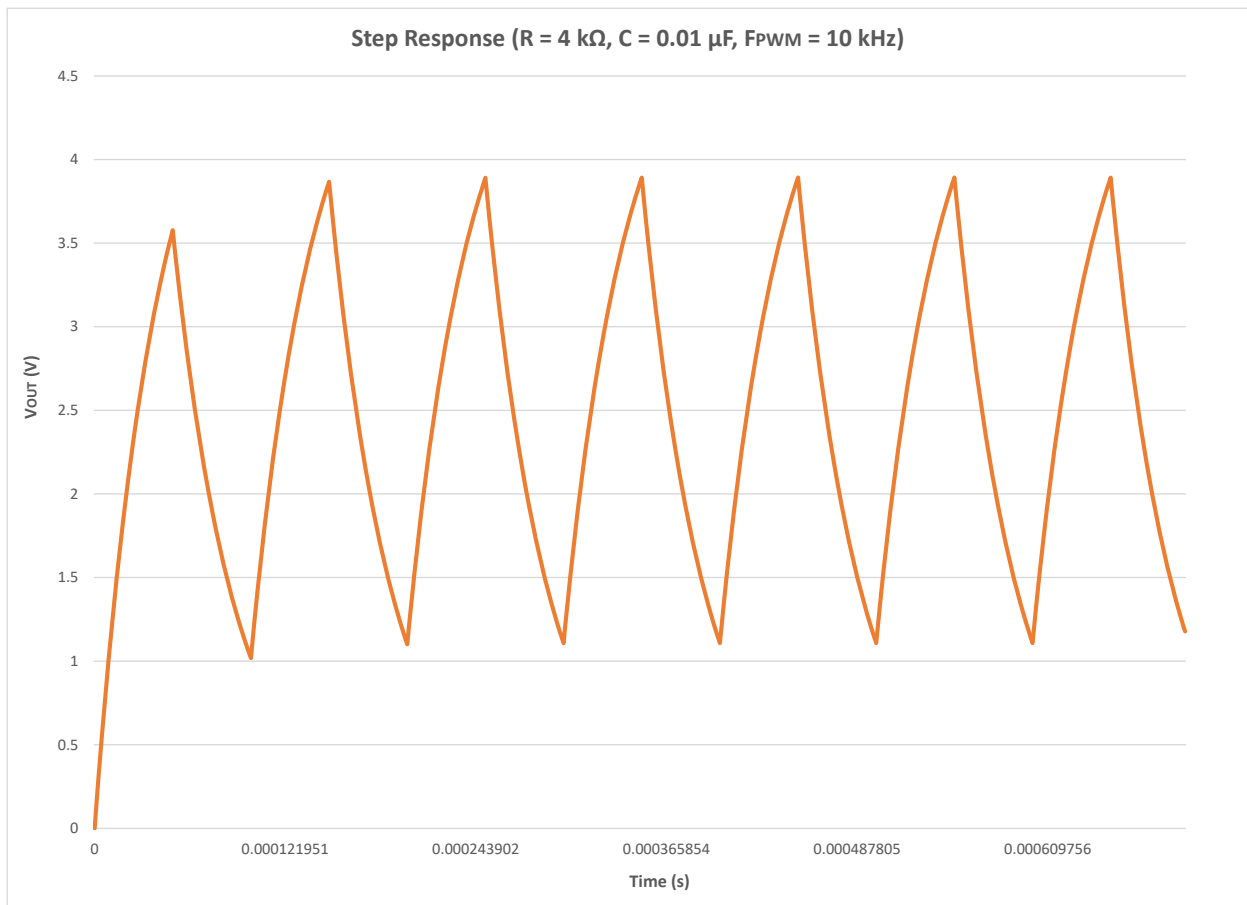


**Figure 2-8. Step Response ( $R = 4\text{ k}\Omega$ ,  $C = 0.01\text{ }\mu\text{F}$ ,  $F_{\text{PWM}} = 100\text{ kHz}$ )**

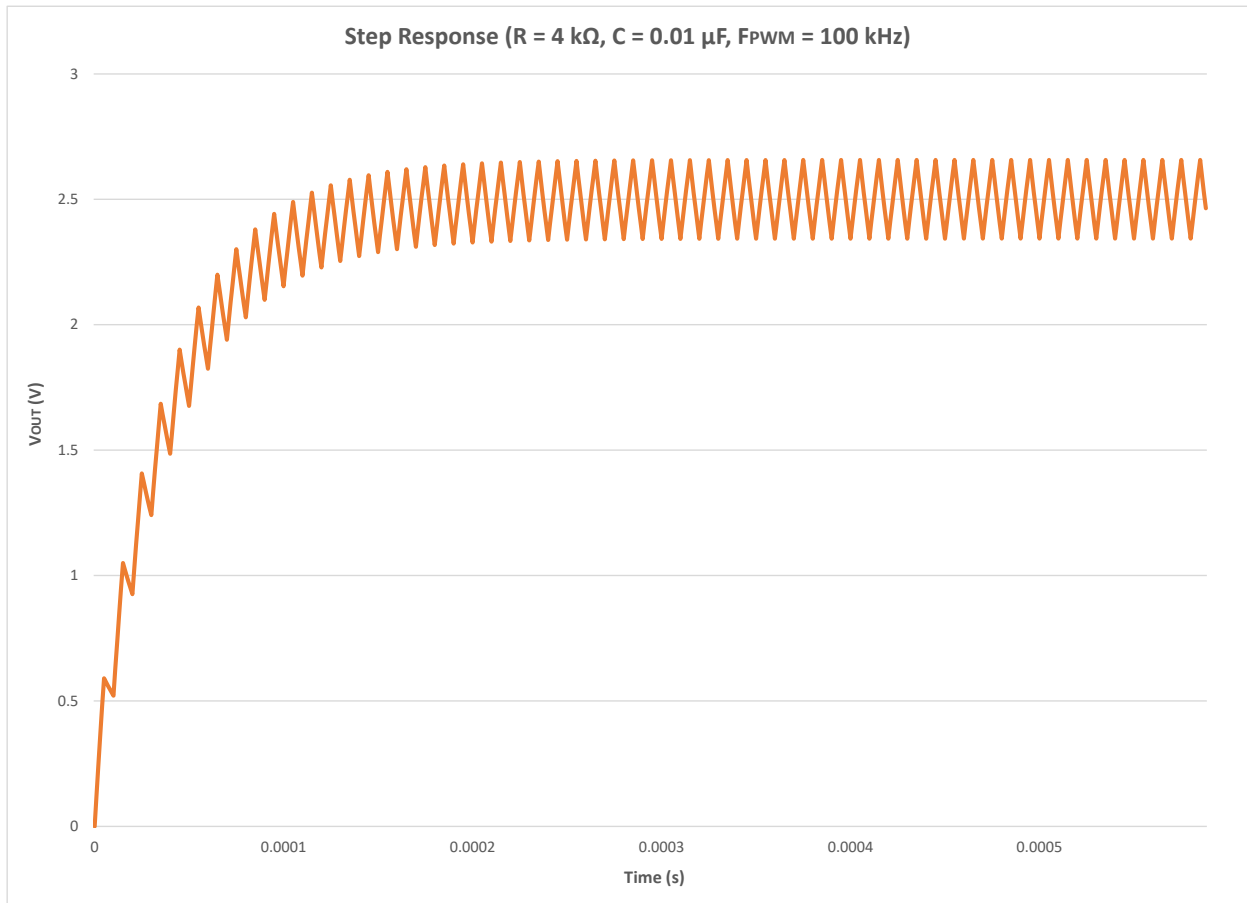

**Figure 2-9. Step Response ( $R = 1.8\text{ k}\Omega$ ,  $C = 0.022\text{ }\mu\text{F}$ ,  $F_{\text{PWM}} = 10\text{ kHz}$ )**



**Figure 2-10. Step Response ( $R = 1.8\text{ k}\Omega$ ,  $C = 0.022\text{ }\mu\text{F}$ ,  $F_{\text{PWM}} = 100\text{ kHz}$ )**

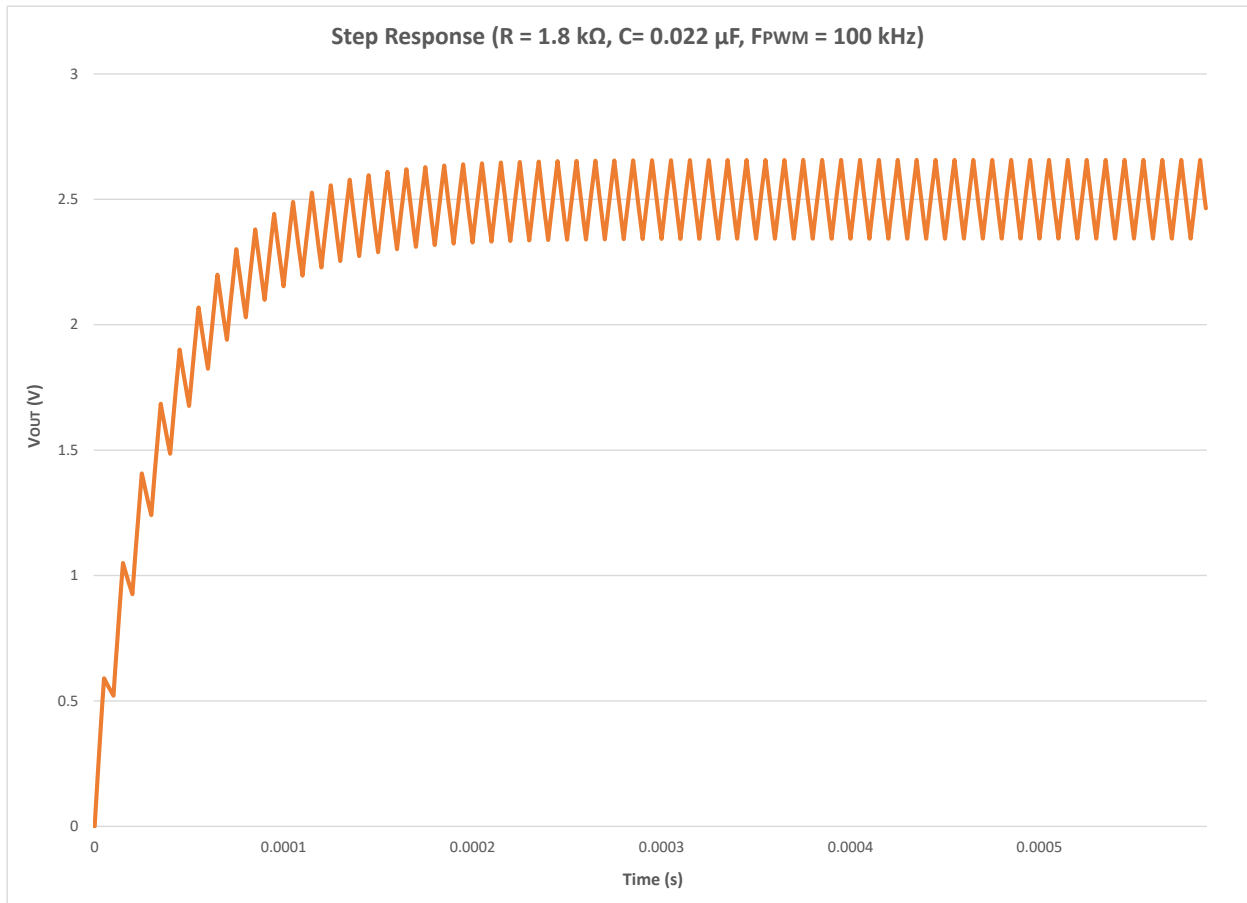

### **3. Conclusion**

PWM signals can be transformed into analog signals using a simple RC type low-pass filter. The PWM duty cycle determines the magnitude of the filter's voltage output. As the duty cycle increases, the average voltage output increases, and vice versa. The PWM frequency determines the amount of attenuation the filter can produce. When the PWM frequency is close to the cut-off frequency, the filter responds quickly, but produces a high amount of ripple in the output signal. As the distance between the cut-off frequency and PWM frequency increases, the response time decreases, but the ripple in the output signal also decreases.

---

## The Microchip Website

---

Microchip provides online support via our website at <http://www.microchip.com/>. This website is used to make files and information easily available to customers. Some of the content available includes:

- **Product Support** – Data sheets and errata, application notes and sample programs, design resources, user's guides and hardware support documents, latest software releases and archived software
- **General Technical Support** – Frequently Asked Questions (FAQs), technical support requests, online discussion groups, Microchip design partner program member listing
- **Business of Microchip** – Product selector and ordering guides, latest Microchip press releases, listing of seminars and events, listings of Microchip sales offices, distributors and factory representatives

---

## Product Change Notification Service

---

Microchip's product change notification service helps keep customers current on Microchip products. Subscribers will receive email notification whenever there are changes, updates, revisions or errata related to a specified product family or development tool of interest.

To register, go to <http://www.microchip.com/pcn> and follow the registration instructions.

---

## Customer Support

---

Users of Microchip products can receive assistance through several channels:

- Distributor or Representative
- Local Sales Office
- Embedded Solutions Engineer (ESE)
- Technical Support

Customers should contact their distributor, representative or ESE for support. Local sales offices are also available to help customers. A listing of sales offices and locations is included in this document.

Technical support is available through the website at: <http://www.microchip.com/support>

---

## Microchip Devices Code Protection Feature

---

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

---

## Legal Notice

---

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with

your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

## Trademarks

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, chipKIT, chipKIT logo, CryptoMemory, CryptoRF, dsPIC, FlashFlex, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Kleer, LANCheck, LinkMD, maXStylus, maXTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PackeTime, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TempTrackr, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, FlashTec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, Vite, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, EtherGREEN, In-Circuit Serial Programming, ICSP, INICnet, Inter-Chip Connectivity, JitterBlocker, KleerNet, KleerNet logo, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, SAM-ICE, Serial Quad I/O, SMART-I.S., SQI, SuperSwitcher, SuperSwitcher II, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, and Symmcom are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2020, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-5224-5851-7

## Quality Management System

For information regarding Microchip's Quality Management Systems, please visit <http://www.microchip.com/quality>.

## Worldwide Sales and Service

AMERICAS	ASIA/PACIFIC	ASIA/PACIFIC	EUROPE
<b>Corporate Office</b> 2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7200 Fax: 480-792-7277 Technical Support: <a href="http://www.microchip.com/support">http://www.microchip.com/support</a> Web Address: <a href="http://www.microchip.com">http://www.microchip.com</a>	<b>Australia - Sydney</b> Tel: 61-2-9868-6733 <b>China - Beijing</b> Tel: 86-10-8569-7000 <b>China - Chengdu</b> Tel: 86-28-8665-5511 <b>China - Chongqing</b> Tel: 86-23-8980-9588 <b>China - Dongguan</b> Tel: 86-769-8702-9880 <b>China - Guangzhou</b> Tel: 86-20-8755-8029 <b>China - Hangzhou</b> Tel: 86-571-8792-8115 <b>China - Hong Kong SAR</b> Tel: 852-2943-5100 <b>China - Nanjing</b> Tel: 86-25-8473-2460 <b>China - Qingdao</b> Tel: 86-532-8502-7355 <b>China - Shanghai</b> Tel: 86-21-3326-8000 <b>China - Shenyang</b> Tel: 86-24-2334-2829 <b>China - Shenzhen</b> Tel: 86-755-8864-2200 <b>China - Suzhou</b> Tel: 86-186-6233-1526 <b>China - Wuhan</b> Tel: 86-27-5980-5300 <b>China - Xian</b> Tel: 86-29-8833-7252 <b>China - Xiamen</b> Tel: 86-592-2388138 <b>China - Zhuhai</b> Tel: 86-756-3210040	<b>India - Bangalore</b> Tel: 91-80-3090-4444 <b>India - New Delhi</b> Tel: 91-11-4160-8631 <b>India - Pune</b> Tel: 91-20-4121-0141 <b>Japan - Osaka</b> Tel: 81-6-6152-7160 <b>Japan - Tokyo</b> Tel: 81-3-6880-3770 <b>Korea - Daegu</b> Tel: 82-53-744-4301 <b>Korea - Seoul</b> Tel: 82-2-554-7200 <b>Malaysia - Kuala Lumpur</b> Tel: 60-3-7651-7906 <b>Malaysia - Penang</b> Tel: 60-4-227-8870 <b>Philippines - Manila</b> Tel: 63-2-634-9065 <b>Singapore</b> Tel: 65-6334-8870 <b>Taiwan - Hsin Chu</b> Tel: 886-3-577-8366 <b>Taiwan - Kaohsiung</b> Tel: 886-7-213-7830 <b>Taiwan - Taipei</b> Tel: 886-2-2508-8600 <b>Thailand - Bangkok</b> Tel: 66-2-694-1351 <b>Vietnam - Ho Chi Minh</b> Tel: 84-28-5448-2100	<b>Austria - Wels</b> Tel: 43-7242-2244-39 Fax: 43-7242-2244-393 <b>Denmark - Copenhagen</b> Tel: 45-4485-5910 Fax: 45-4485-2829 <b>Finland - Espoo</b> Tel: 358-9-4520-820 <b>France - Paris</b> Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79 <b>Germany - Garching</b> Tel: 49-8931-9700 <b>Germany - Haan</b> Tel: 49-2129-3766400 <b>Germany - Heilbronn</b> Tel: 49-7131-72400 <b>Germany - Karlsruhe</b> Tel: 49-721-625370 <b>Germany - Munich</b> Tel: 49-89-627-144-0 Fax: 49-89-627-144-44 <b>Germany - Rosenheim</b> Tel: 49-8031-354-560 <b>Israel - Ra'anana</b> Tel: 972-9-744-7705 <b>Italy - Milan</b> Tel: 39-0331-742611 Fax: 39-0331-466781 <b>Italy - Padova</b> Tel: 39-049-7625286 <b>Netherlands - Drunen</b> Tel: 31-416-690399 Fax: 31-416-690340 <b>Norway - Trondheim</b> Tel: 47-72884388 <b>Poland - Warsaw</b> Tel: 48-22-3325737 <b>Romania - Bucharest</b> Tel: 40-21-407-87-50 <b>Spain - Madrid</b> Tel: 34-91-708-08-90 Fax: 34-91-708-08-91 <b>Sweden - Gothenberg</b> Tel: 46-31-704-60-40 <b>Sweden - Stockholm</b> Tel: 46-8-5090-4654 <b>UK - Wokingham</b> Tel: 44-118-921-5800 Fax: 44-118-921-5820